

Q1) a-Using RTD PT100 for temperature range (22C to 190C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_s=9V$, $R_1=200\Omega$).

b-If we will send the sensor output for a distance with same voltage reference.

c-What is the ADC digital output if the temperature is 100C.

d-What is the temperature if the ADC output is (10011110).

$$red = 2V \quad [14 \text{ pts}]$$

Q2) Using Acceleration sensor (sensitivity = $0.4mA/g$), with offset $7mA @ 0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor = $4V/6KHz$).


a-Draw the block diagram of the operation.

b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c-What is the value of the output of the counter if the acceleration is $-0.5g$. [10 pts]

Q3) Barometer sensor sensitivity is $5mV/bar$, and $5\Omega/cm$ pot. level sensor for 150cm range used for measuring level ($V_s=9V$ use, $R_1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values. [10 pts]

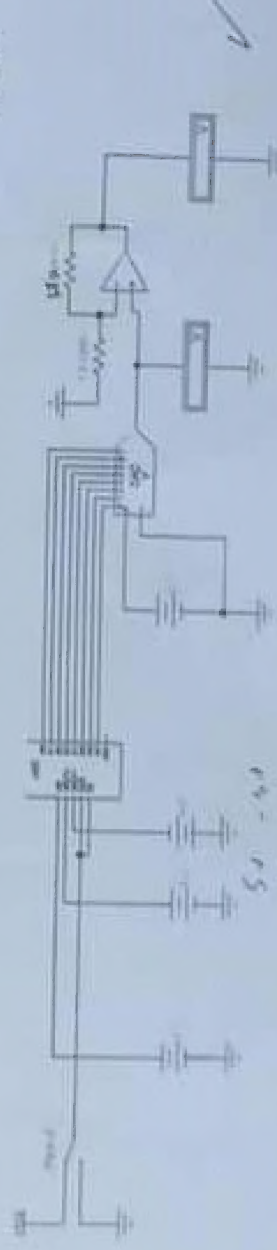Q4) What is the value of voltmeters and ADC and DAC outputs. [8 pts]



Q5) a- Using Thermocouple sensor Type K with $0C$ reference, What is the value of temperature if its output is $19mV$, What is its output at the temperature $V_{K10}(-40C)=?$. [8pts]

Q1.a) A liquid level sensor has an input range of 0 to 15cm. Use the calibration results given in the table to estimate the maximum hysteresis as a percentage of f.s.d.

Liquid h cm	0	1.5	3	4.5	6	7.5	9	10.5	12	13.5	15
Output volts h increasing	0	0.35	1.42	2.4	3.43	4.35	5.61	6.5	7.77	8.88	10.2
Output volts h decreasing	0.14	1.25	2.32	3.55	4.43	5.7	6.78	7.8	8.87	9.65	10.2

Q1.b) A temperature sensor has a span of 20.250C. A measurement results in a value of 55C for the temperature. Specify the error if the accuracy is:

- 1- $\pm 0.5\%$ fs 2- $\pm 0.75\%$ of span 3- $\pm 0.8\%$ of reading

What is the possible temperature in each case?

(6 pts)

Q2.a) Drive the equation of the bridge offset voltage for the current balance bridge?

Q2.b) Design a high-pass RC filter that must drive 120Hz noise down to 1% using a capacitor 0.01 μ F. Specify the attenuation of a 30KHz signal?

Q2.c) Signal conditioning analysis showing that the following equation must relate output voltage to input voltage: $V_o = 3.35V_{in} + 2.68$

Design circuits to do this using (a) a summing amplifier (b) a differential amplifier?

(8 pts)

Q3.a) A 12-bit bipolar DAC has a 10V reference

- 1- What output voltage results from digital input of 4A6 H.

- 2- An output of 4.74V is needed. What digital input would come closest to this value? By what percentage is the actual output different?

Q3.b) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

(6 pts)

Good Luck

$$V_o = \frac{R_f}{R_A} (V_{in} - V_{ref})$$

$$V_o = \frac{R_f}{R_A} \sqrt{V_{in}} - \frac{R_f}{R_A} \sqrt{V_{ref}}$$

$$\frac{V_o}{R_f} = \frac{1}{R_A} \sqrt{V_{in}} - \frac{1}{R_A} \sqrt{V_{ref}}$$

EE443

Q1) Temperature sensor sensitivity is $4\Omega/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280Ω . Using Wheatstone bridge convert its range to volt, and send its value using (4mA $\pm 20\text{mA}$ transmitter) and prepare it for 8bit ADC with voltage reference $0.5V_{\text{ref}}$.
a) What is the digital output of ADC at the temperature -2°C . [12 pts] (33)d

Q2) Accelerometer sensor sensitivity is 0.33mA/g , used for measuring Acceleration in the range $(\pm 20\text{g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$. [10 pts] 103 or 106

a) What is the digital output of ADC at the acceleration is -3g .
b) What is the acceleration when the digital output is 06H. -13 or 6(12, 16)

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference $(0-5V)$, where: sensor output range $(-150 - +150\text{mV})$ with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal. [10 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	107.6	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can). [4 pts]

Q1.a) An alarm light goes ON when a pressure sensor voltage rises above 4.00 V. The pressure sensor outputs 20 mV/kPa and has a time constant of 4.9 s. How long after the pressure rises suddenly from 100 kPa to 400 kPa does the light go ON?

Q1.b) A load cell is calibrated at $21\epsilon^{\theta}$ and has the following deflection/load characteristic:

Load(kg)	0	50	100	150	200
Deflection (mm)	0	1	2	3	4

When used at $35\epsilon^{\theta}$, its characteristic changes to the following:

Load(kg)	0	50	100	150	200
Deflection (mm)	0.2	1.3	2.4	3.5	4.6

Determine the sensitivity coefficients

(10 pts)

Q2.a) A measurement signal has a frequency less than 1KHz, but there is unwanted noise at about 1MHz. Design a filter that attenuate the noise to 1% using a capacitor $0.01\mu\text{f}$. What is the effect on the measurement signal at its maximum of 1KHz (give a comment on the result)?

Q2.b) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_{in} - 2.68$. Design circuits to do this using a differential amplifier?


(12 pts)

Q3.a) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

Q3.b) Design a 5-bit weighted-resistor DAC whose full-scale output voltage is -15v. Logic levels are 1=5v and 0=0v. What is the output voltage when the input is 01010?

(10 pts)

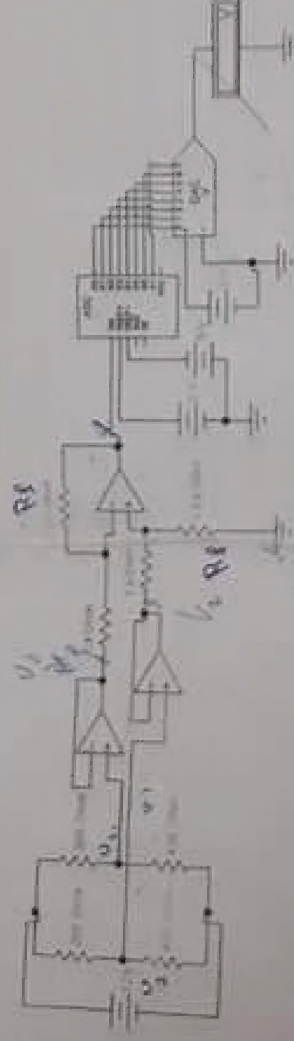Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.



Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal (give the 3 attempts with comments).

Q3) using accelerometer which sensitivity 0.3mA/g, and using $R=2000\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V, sampling time 0.1sec:

- Draw the block diagram of the operation
- What is the digital output (in binary) if the acceleration is 11g.
- What is the value of acceleration if the digital output is $(190)_{10}$

Good Luck (Zeyad Hamza)

Handwritten notes and calculations:

Block diagram of the operation:

```

    graph LR
        Acc[Accelerometer] --> VFC[Voltage-to-Frequency Converter]
        VFC --> ADC[ADC]
        ADC --> DAC[Digital-to-Analog Converter]
        DAC --> Out[Output]
    
```

Calculations:

For 11g acceleration:

$$V = 11g \times 0.3mA/g = 3.3mA$$

$$f = 3.3mA \times 5KHz/V = 16.5KHz$$

For digital output (190)₁₀:

$$V = \frac{190}{256} \times 5V = 3.71V$$

$$f = 3.71V \times 5KHz/V = 18.55KHz$$

$$T = \frac{V_{SD}}{V_{SD}}$$

Q1) a- Using RTD PT100 for temperature range (25°C to 190°C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_S=9V$, $R1=200\Omega$).

b- If we will send the sensor output for a distance with same voltage reference.

c- What is the ADC digital output if the temperature is 100°C.

d- What is the temperature if the ADC output is (10011110).

[14 pts]

Q2) Using Acceleration sensor (sensitivity $-0.14mV/g$), with offset $7mA @ 0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor $4V/6KHz$).

a- Draw the block diagram of the operation.

b- Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c- What is the value of the output of the counter if the acceleration is $-0.5g$.


[10 pts]

Q3) Barometer sensor sensitivity is $5mV/bar$, and $5\Omega/cm$ pot. level sensor for 150cm range used for measuring level ($V_S=9V$ use, $R1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm) and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]


Q4) What is the value of voltmeters and ADC and DAC outputs.

[8 pts]

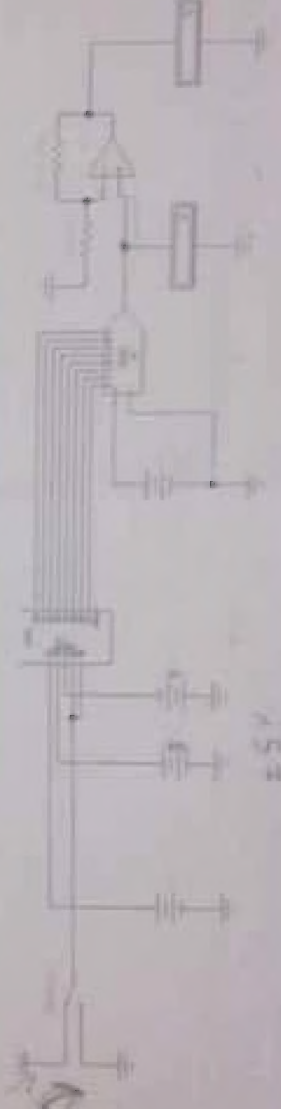

Q5) a- Using Thermocouple sensor Type K with 0°C reference, What is the value of temperature if its output is 19mV, What is its output at the temperature $V_{K19}(-40°C)=?$ [8pts]

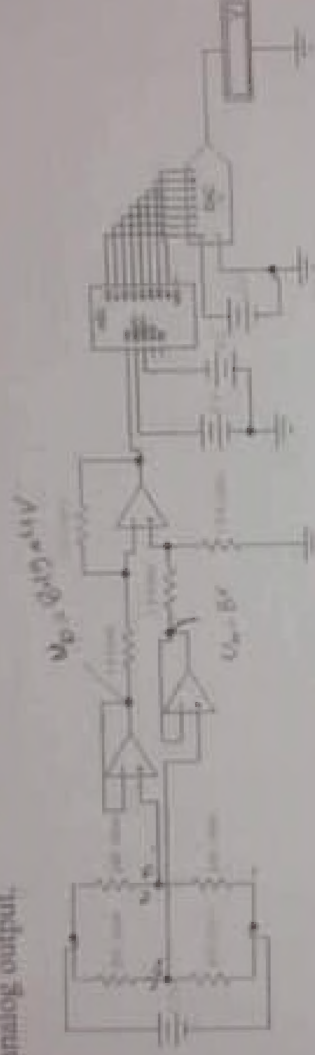Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.



Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal(give the 3 attempts with comments)

Q3) using accelerometer which sensitivity 0.3mA/g , and using $R=200\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V , sampling time 0.1sec :

- Draw the block diagram of the operation
- What is the digital output (in binary) if the acceleration is 11 g.
- What is the value of acceleration if the digital output is (190)₁₀

University of Tripoli – Faculty of Engineering
Electrical & Electronic Engineering Department

EE463 1st Exam Time: 1: 30 hr spring 2018 20/12/2018

Q1) What elements of data acquisition system, explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$, for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC (V_{ref} $0-4 \text{ V}$).


B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

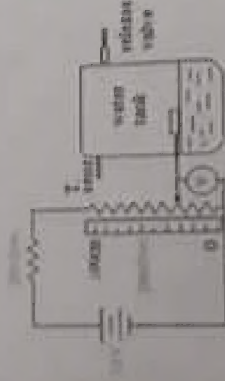Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$), RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar .



Good Luck (Zeyad Hamza)

- Q1) a- What is the meaning of single ended signal, differential signal and give example. [6 pts]
b- What is sample and what is hold and when we use them. [6 pts]

Q2) Using Temperature sensor (RTD-PT100), in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R1=110$, $R2=120$), and using voltage to frequency converter VFC (scale factor = $10\text{KHz}/1.12V$).

- a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.
b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is 110C. 552
c- Draw Block diagram of the circuit. [16 pts]

Q3) An accelerometer sensor sensitivity is 0.145mV/g , used for measuring pressure in the range ($\pm 20\text{g}$), and the value of its output @ 0g is 5.2mA , using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

- a) Calculate sensor output range (current, voltage, Binary).
b) What is the digital output of ADC at the acceleration is 8g .
c) What is the value of acceleration when the digital output is 0DH.92H. [15 pts]
d) If the frequency of the signal is 120Hz and there is unwanted noise with frequency 15KHz , design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range. [05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 12.4°C .

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	103.6	105.1	106.3	107.1	108.3

[08 pts]

D) (10011110) = 158 $V_o = D_o \Delta = 1.8515625V$

$V_{in} = \frac{V_o \times 10^{11}}{R} = 3.797362007V$


$R_{TD} = \frac{V_o \times R}{V_s - V_o} = 145.9783291\Omega$

$T = \frac{R_{TD} \times 100}{0.39} = 117.8931516^\circ C$

b) we use (4-20) mA transmitter where its Voltage range is (1-5)V and the output from the Voltage Divider circuit is suitable and in range of use.

Q2. Acceleration $S = 0.14 \text{ mA/g}$ @ $D_g = 7 \text{ mA} \pm 30g$

Use VFC (4V/6 kHz) = 1.5 kHz

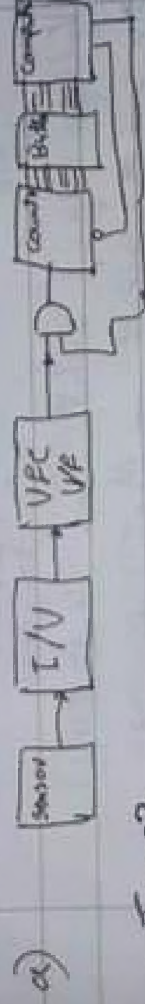

$T_{0.02}$

Range (-30g

+30g)

$(7 \text{ mA} + 0.19330 \times 2.8 \text{ mA}) \quad 7 + 0.14 \times 30 = 11.2 \text{ mA}$

assume $R = 100\Omega$


$V_o = IR \Rightarrow (0.28 \sim 1.12)V$

output from VFC = 0.28×1.5 1.12×1.5

= (420 Hz) 1680 Hz

Control output range = $((420 \times 0.2))$ (1680×0.2)

(84) 336

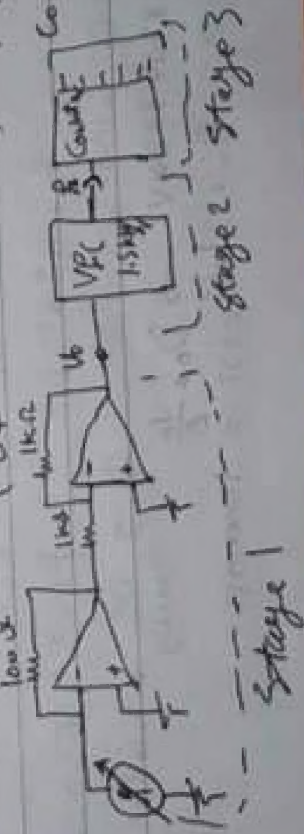

Spring 2018

Q1: Single ended signal is a constant output signal depends on the parameters of the circuit & differential signal is a difference signal at the output between two terminals in a bridge.

We use sample and hold because ADC needs a finite amount of time to measure the signal voltage.

Q2: 5 mV/K , $(30-120)^\circ\text{C}$ V_{TC} 0.5 kHz/V f_s 10 Hz
 $T = 0.1 \text{ s}$

Voltage range $(30 \times 5 \text{ mV/K} = 150 \text{ mV})$ $120 \times 5 \text{ mV} = 600 \text{ mV}$

Frequency range $(150 \times 0.5 = 75 \text{ Hz})$ $600 \times 0.5 = 300 \text{ Hz}$

Counter range $(75 \times 0.1 = 7.5 = 7)$ $300 \times 0.1 = 30$

For Temperature 112°C $V_o = 112 \times 5 \text{ mV/K} = 560 \text{ mV}$

$V_{TC} = 0.5 \times 560 = 280 \text{ Hz}$, $C_o = 280 \times 0.1 = 28$ ✖

Q3: 0.13 mA/bar range $\pm 20 \text{ bar}$ \odot $0.01 \text{ bar} = 1 \text{ mV}$ $R = 150$

Using bipolar ADC 8 bit $\pm 4 \text{ V}$

Amplitude range $(-20 \times 0.13 \text{ mA} = -2.6 \text{ mA})$ $\sim (20 \times 0.13 \text{ mA}) = 2.6 \text{ mA}$

Voltage range $(1.4 \times 150 = 210 \text{ mV})$ $\sim 6.6 \times 150 = 990 \text{ mV}$

$-4 = 0.210 \text{ M} + \text{offset}$ $M = \frac{400}{39}$ $V_o = M V_{in} + \text{offset}$

$+4 = 0.99 \text{ M} + \text{offset}$ $\text{offset} = -\frac{80}{13}$ $D = \frac{8}{2^8} = \frac{1}{32}$

a) in 8 bar find $D_o \Rightarrow ((8 \times 0.13) \times 4) \times 150 = 756 \text{ mV}$

$V_o = \frac{400}{39} \times 0.756 - \frac{80}{13} = 1.6$

$D_o = \frac{1.6 \times 10^4}{5.6132} = 179.7 \approx 179 = (10110011)_2$ ✖

Q1) What elements of data acquisition system explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$, for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC ($V_{ref} = 0-4 \text{ V}$)

B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$) , RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp) is more than 49°C or pressure is more than 10 bar or level is less than 33 cm

B- Turn ON release valve if pressure is more than 15 bar .



Q1) What elements of data acquisition system. explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$ for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC (Vref $0-4 \text{ V}$).

B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$) , RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar .



ET 303

Q1.a) An ADC that will encode pressure data is required. The input signal is 666.6 mV/pa and a resolution of 0.5 pa is required. find the number of bits necessary for the ADC. The reference is 10.0 V

b) find the maximum measurable pressure?

Q1.b) An 8-bit DAC with a 3.00 V reference connects to a light source with an intensity given by $I = 10 - 0.1 \text{ mW/cm}^2$. What intensities are produced by digital inputs of 1111, 7111? (18 pts)

Q2.a) Describe the working principle of thermocouple sensors. What are techniques employed for reference junction compensation?

Q2.b) An RTD has $\alpha = 0.005/^\circ\text{C}$, $R_0 = 500 \Omega$, and a dissipation constant of $P_D = 30 \text{ mW/}^\circ\text{C}$ at 20°C . The RTD is used in a bridge circuit with $R_1 = R_2 = 500 \Omega$ and R_3 a variable resistor used to null the bridge. If the supply is 10 V and the R_3 is placed in a bath at 0°C , find the value of R_3 to null the bridge. (12 pts)

Q2.c) A resistive element of a wire-wound pot is made from 10 m of $100 \Omega/\text{m}$ resistance and is wound as a coil of 200 loops. the range of the pot is 350 degree. What is the resolution of this pot? (12 pts)


Q3.a) Describe the working principle of linear variable differential transformer?

Q3.b) A strain gauge has $GF = 2.06$ and $R = 120 \Omega$, and is made from wire with $\alpha = 0.0034/^\circ\text{C}$ at 25°C . The dissipation factor is given as $P_D = 25 \text{ mW/}^\circ\text{C}$. What is the maximum current that can be placed through the SG, to keep self-heating errors below 1 micro-strain? (12 pts)

Q3.c) Water is pumped through a 1.5 m diameter pipe with a flow velocity of 2.50 m/s . Find the volume flow rate and weight flow rate. The weight density is 62.4 lb/ft^3 . (12 pts)

$$\Phi = AV$$

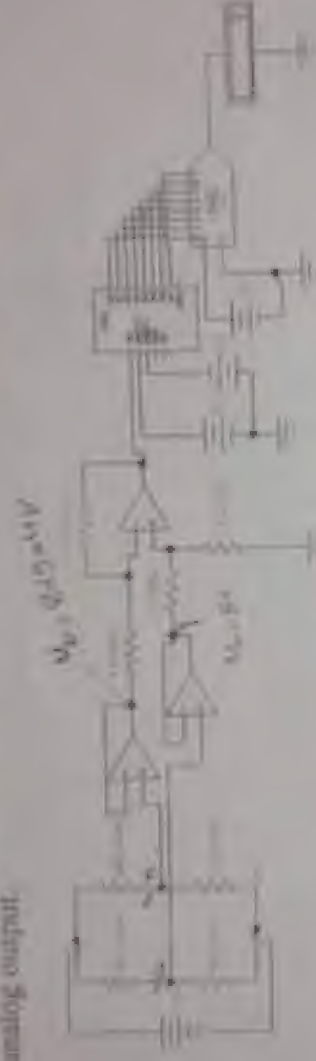Q1) From the circuit below what is the value of ADC digital outputs and DAC analog output.



Q2) A measurement signal has a frequency 800Hz, but there is unwanted noise at about 10KHz. Design filter that attenuate noise as possible with better effect on the signal (give the 3 attempts with comments).

Q3) using accelerometer which sensitivity 0.3mA/g , and using $R=200\Omega$ for voltage conversion, and using VFC which scale factor 5KHz/V , sampling time 0.1sec :

- Draw the block diagram of the operation
- What is the digital output (in binary) if the acceleration is 1g .
- What is the value of acceleration if the digital output is $(190)_{10}$.

12/2/2019

EE463

- Q1) a- Using RTD PT100 for temperature range (22C to 190C), design a signal conditioning circuit for (0-3V) ADC. (use voltage divider circuit, $V_s=9V$, $R_1=200\Omega$).
b- If we will send the sensor output for a distance with same voltage reference.
c- What is the ADC digital output if the temperature is 100C.
d- What is the temperature if the ADC output is (10011110).

$$V_{out} = 2V \quad (14 \text{ pts})$$

- Q2) Using Acceleration sensor (sensitivity $= 0.14 \text{ mA/g}$), with offset 7 mA/0g , for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor $= 4V/6KHz$).
a- Draw the block diagram of the operation.
b- Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.
c- What is the value of the output of the counter if the acceleration is $-0.5g$.


(10 pts)

- Q3) Barometer sensor sensitivity is 5 mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150cm range used for measuring level ($V_s=9V$ use, $R_1=150\Omega$). Design circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values.

(10 pts)

- Q4) What is the value of voltmeters and ADC and DAC outputs.

(8 pts)

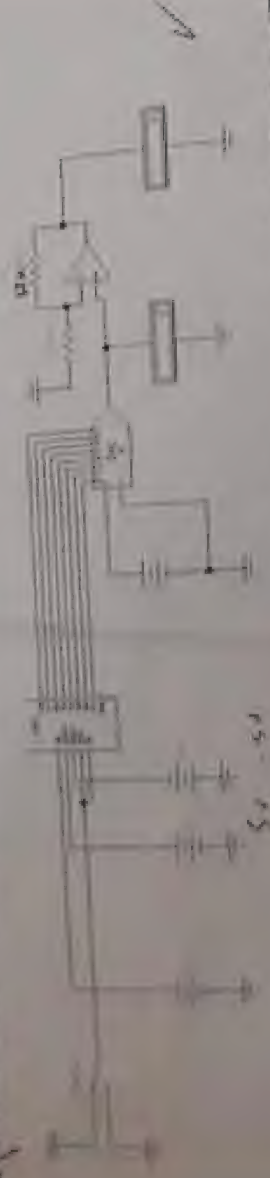

- Q5) a- Using Thermocouple sensor Type K with DC reference, What is the value of temperature if its output is 19mV. What is its output at the temperature $V_{ref}(-40C)=7.18 \text{ mV}$.

Good Luck (Zeyad)

52012

Q3 b) $0.25 \Rightarrow f_c \sqrt{\frac{1501}{\sin^2 - 1}} = 10\sqrt{15} = 38.7284 \text{ Hz}$

the effect of filter on the signal

$\frac{1}{\sqrt{1 + (\frac{1501}{\sin^2})^2}} = \frac{1}{93.025} = 0.01075$ ~~Very good signal~~ ~~the filter should be~~

Assume (HFE)

$\Rightarrow f_c \sqrt{\frac{8^2 - 2^2 4^2}{1501}} = \sqrt{\frac{140^2 - 0.025^2 1501}{0.1511}} = 580.947 \text{ Hz}$

Effect of filter on the signal


$\frac{1}{\sqrt{1 + (\frac{1501}{\sin^2})^2}} = 2.58284 \%$

Q4 a, b \rightarrow dis. ge

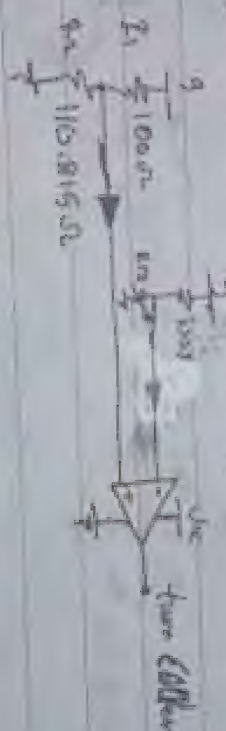c) RTD with linear Approximation find R_{0130}°

$\alpha_0 = \frac{1}{R_0} \left(\frac{R_0 - R_0}{T_0 - T_0} \right) = \frac{1}{110.2} \left(\frac{111.7 - 107.6}{20 - 0} \right) = \frac{41}{22040} \text{ } ^\circ\text{C}^{-1}$

$R_0 R_0 [1 + \alpha_0 \Delta T] = 110.2 [1 + \frac{41}{22040} (15 - 10)] = 110.815$



Q5 from notebook *

Q1) What elements of data acquisition system. explain two of them

Q2) Temperature sensor which sensitivity = $0.11 \text{ mA}/^\circ\text{C}$, and its value @ $0^\circ\text{C} = 5 \text{ mA}$ for temperature range ($\pm 40^\circ\text{C}$), and using $R = 150 \Omega$ for converting to volt, voltage supply 12 V .

A- Design circuit to send the sensor output for long distance and for ADC (Vref $0-4 \text{ V}$).

B- What is the digital output of ADC if the temperature is 33°C , -14°C ?

C- What is the temperature if the digital output is 88H?

Q3) Sensor used to measure pressure in range ($0-30 \text{ bar}$) with sensitivity ($7 \text{ mV}/\text{bar}$) , RTD PT100 to measure temperature, potentiometer used to measure the level as shown in figure.

A- Design circuit to turn ON buzzer if (temp is more than 49°C or pressure is more than 10 bar or level is less than 33 cm)

B- Turn ON release valve if pressure is more than 15 bar .



Spring 2017

Q1. 4.5V $\pm 20\%$ Use Bridge and then 4-bit ADC and then 8-bit ADC 0-5V



$$V_{\text{avg}} \pm 25\% \left((-25 \times 4) + 250 + 180\Omega \sim (25 \times 4) + 280 + 380\Omega \right)$$

Using Bridge with R_1, R_2, R_3, R_4

$$V_A = 9 \times \frac{180}{180+380} = 4.5V \quad V_B = 9 \times \frac{180}{180+380} = 4.5V$$

at nulling $V_{AS} = 0V$ *

$$\text{at maximum } V_0 = 9 \times \frac{380}{180+380} = 6.107142852V$$

$$V_{AB} = 1.607142857V$$


$$V_{\text{avg}} (0 \sim 1.607142852V)$$

Using summing circuit to add the output of sensor with 1 output range $(1 \sim 2.607142852V)$


We need SC for ADC

$$M = \frac{28}{9}$$
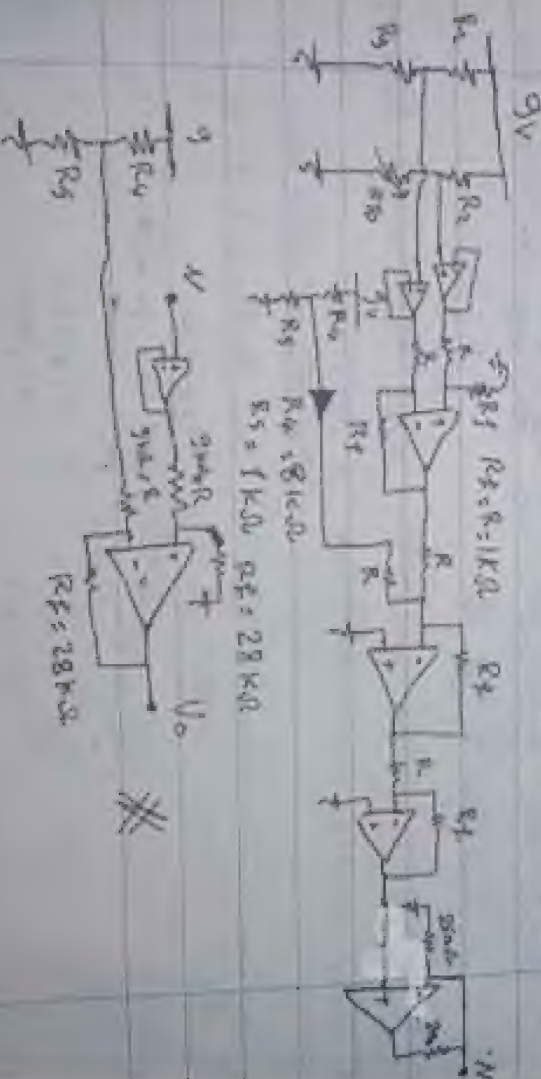
$$D = (M + offset) \quad offset = -\frac{28}{9} \quad V_0 = \frac{28}{9} (V_A - 1)$$



Supper Notepad

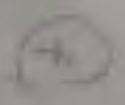

EE46A

Q1) Temperature sensor sensitivity is $4\text{ mV}/^\circ\text{C}$ in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 28 mV . Using Wheatstone bridge convert its range to volts , and send its value using $(4\text{ mA } 20\text{ mA transmitter})$ and prepare it for 8 bit ADC with voltage reference 0.5 Vref .

a) What is the digital output of ADC at the temperature -2°C [12 pts] (33) d

Q2) Accelerometer sensor sensitivity is $0.33\text{ mV}/\text{g}$ used for measuring Acceleration in the range $(\pm 20\text{ g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{ V}$.

100 or 1000

a) What is the digital output of ADC at the acceleration is -3 g .

b) What is the acceleration when the digital output is 06 H . [12 pts] (17) (17.5)

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0.5 V) , where sensor output range $(-150 \rightarrow +150\text{ mV})$ with frequency 15 Hz . Noise signal 20 mV with frequency 150 Hz , and design filter that Attenuate the noise signal to 25 mV , and taking in account the effect of the filter on the sensor signal. [16 pts]

Q4) Using Thermocouple sensor Type J with 0°C reference find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature ($^\circ\text{C}$)	0	8	10	18	26
Resistance (Ω)	107.4	109.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Q1) Temperature sensor sensitivity is $0.42\text{mA}/^{\circ}\text{C}$, used for temperature range ($\pm 50^{\circ}\text{C}$).

Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.


a) What is the digital output of ADC at the temperature 31°C , -20°C .

b) What is the temperature when the digital output is B6H. (10 pts)

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference ($0-10\text{V}$), where: sensor output range ($-100 \sim +100\text{ mV}$) with frequency 25Hz , Noise signal 20mV with frequency 260Hz , and using filter that Attenuate the noise signal to 20% of its value, and taking in account the effect of the filter on the sensor signal. (10 pts)

Q3) Using pressure sensor which sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\text{mV}/^{\circ}\text{C}$ and its value at zero $^{\circ}\text{C}$ $= 300\text{mV}$. Design circuit which open Valve when the pressure is more than 15bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. (10 pts)

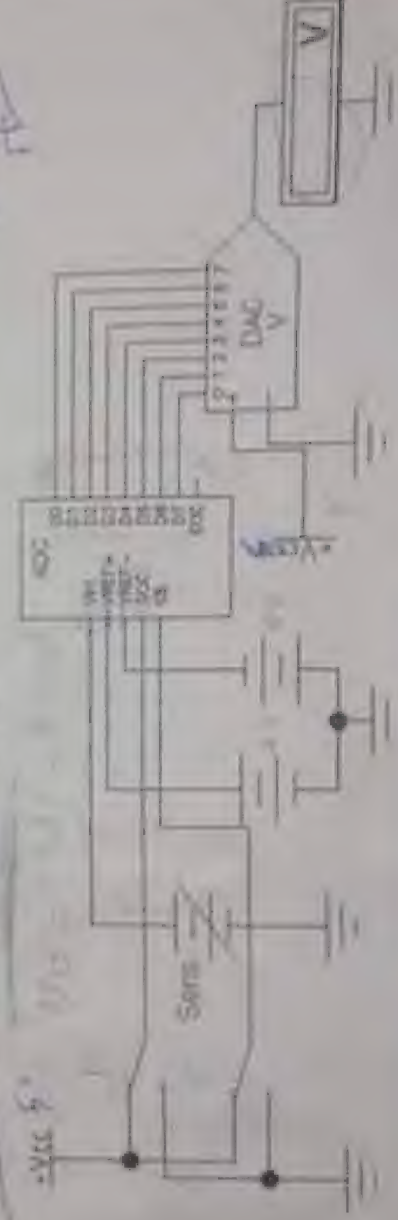Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C and -30°C . Where: sensor sensitivity $= 15\text{mV}/^{\circ}\text{C}$, sensor output at $0^{\circ}\text{C} = 100\text{mV}$, sensor range $= \pm 50^{\circ}\text{C}$. (10 pts)



17.6.2018 13:16:18

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

EE463 Final Exam Time: 2 hr Spring 2017 3/2/2018

Q1) Temperature sensor sensitivity is $4\text{ mV}/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280 mV . Using Wheatstone bridge convert its range to volts , and send its value using 4 mA $\pm 20\text{ mA}$ transmitter, and prepare it for 8 bit ADC with voltage reference $0-5\text{Vref}$.
a) What is the digital output of ADC at the temperature -2°C . [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33 mA/g , used for measuring Acceleration in the range $(\pm 20\text{ g})$. Design signal condition circuit for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

a) What is the digital output of ADC at the acceleration is -3 g . [12]
b) What is the acceleration when the digital output is 0011 . [4] [12 pts]

Q3) Design the signal conditioning circuit to connect the sensor to 10 bit ADC with voltage reference $(0-5\text{V})$, where sensor output range $(-150) - (+150\text{ mV})$ with frequency 15Hz . Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal. [10 pts]

$$\left(\frac{V_o}{V_i}\right) = \frac{1}{1 + j\omega RC}$$

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 17°C and design circuit operate heater if the temperature is less than 13°C . [12 pts]

Temperature $(^\circ\text{C})$	6	9	100	15	20
Resistance (Ω)	107.5	108.1	110.2	111.3	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zeyad)

b) 0.184 find P $184 = 24$

$$V_o = (24 \times 0.184) = 4.416 \Rightarrow V_{in} = \frac{V_o \times 100}{M} = 0.283125V$$

$$I = \frac{V_{in}}{R} = \frac{1.8875}{100} = 1.8875 \text{ mA}$$

$$P = \frac{(1.8875 \times 4)}{100} = 16.25 \text{ mW}$$

Q4. DAC in (01010101) = 85, $D = \frac{7}{8} = \frac{1}{100}$

$$V_{o1} = \frac{85}{100} = 0.85$$

$$V_{o2} = V_{o1} \times 2.7 = 1.7925$$

$$D_o \Rightarrow D = \frac{5}{256} = \frac{5}{256}, D_o = \frac{V}{D} = 91.8, 91 + 1.6111011$$

Q5. a)

b) RTO find Quadratic Approximation then find @ 11.4

$$107.6 = 110.2(1 + \alpha_1(0.10) + \alpha_2(0.10)^2) \Rightarrow 1$$

$$111.7 = 110.2(1 + \alpha_1(20.10) + \alpha_2(20.10)^2) \Rightarrow 2$$

$$-10\alpha_1 + 100\alpha_2 = \frac{13}{531}$$

$$10\alpha_1 + 100\alpha_2 = \frac{15}{1102}$$

$$\alpha_1 = \frac{41}{22000}$$

$$\alpha_2 = \frac{11}{220000}$$

$$R = 110.2(1 + \alpha_1(11.4 - 10) + \alpha_2(11.4 - 10)^2) = 110.47622 \Omega$$

Q1.a) 1- Explain what is meant by active and passive sensor?

2- State the tasks of signal conditioning?

3- Using block diagrams, describe a data acquisition system?

Q1.b) An instrument measures resistance from 0 to 1500Ω . What is the uncertainty in an indicated measurement of 397Ω if instrument has an accuracy of (a) $\pm 0.5\%$ of FS (b) $\pm 0.5\%$ of span? (12 pts)

Q2.a) A current balance bridge has $R_1=R_2=10K\Omega$, $R_3=1K\Omega$, $R_4=950\Omega$, $R_5=50\Omega$, $V_s=10V$, and a high-impedance null detector. Find the current required to null the bridge if R_4 changes by 1Ω ?

Q2.b) An air conditioning should come on when the sum of the temperature and humidity sensor voltages does above $1V$. A threshold circuit in the air conditioner requires $5V$ for turn-on. Design an interface circuit to connect the two sensors to the air conditioning unit? (10 pts)

Q3.a) For the following circuit:



1- Explain the behavior of the circuit when the frequency of the source changes from zero to infinity?

2- Derive the expressions of the transfer function and the cutoff frequency?

Q3.b) A displacement sensor has an input range of 0 to 5cm and a standard supply voltage $V_s=0.5V$. Using the calibration results in the table, estimate the sensitivity coefficients associated with supply voltage variations?

Input x (cm)	0	0.5	1	1.5	2	2.5	3
Output V (mV, $V_s=0.5$)	0	16.5	32	44	51.5	53.5	58
Output V (mV, $V_s=0.6$)	0	21	41.5	56	65	70.5	74

(10 pts)

Good Luck

$$\sqrt{(\partial V / \partial x)^2 + (\partial V / \partial V_s)^2}$$

EE463 33-34 8-9 2.1

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department

Final Exam Time: 2 hr Spring 2017 3/2/2018

EE463

Q1) Temperature sensor sensitivity is $4\text{ mV}/^\circ\text{C}$, in the range $(\pm 25^\circ\text{C})$ and its value at 0°C is 280 mV . Using Wheatstone bridge convert its range to Volts, and send its value using 4 mA $\pm 20\text{ mA}$ transmitter, and prepare 0 for 8bit ADC with voltage reference 0.5Vref
a) What is the digital output of ADC at the temperature -2°C [12 pts]

Q2) Accelerometer sensor sensitivity is 0.33 mV/g , used for measuring Acceleration in the range $(\pm 20\text{ g})$. Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4\text{V}$.

- a) What is the digital output of ADC at the acceleration is -3 g [7]
b) What is the acceleration when the digital output is 06H [14] [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0.5V) , where sensor output range $(-150 \text{ to } +150\text{ mV})$ with frequency 150 Hz . Noise signal 20 mV with frequency 150 Hz , and design filter that Attenuate the noise signal to 25 mV , and taking in account the effect of the filter on the sensor signal. [10 pts]

$$V_s = V_r \cdot \frac{1}{1 + j\omega RC}$$

Q4) Using Thermocouple sensor Type J with 0°C reference, find the value of its output at 32°C . Design circuit to operate cooler if the temperature is more than 32°C , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at 13°C and design circuit operate heater if the temperature is less than 13°C .

Temperature $(^\circ\text{C})$	0	5	10	15	20
Resistance (Ω)	107.5	109.1	110.7	112.3	113.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zeyad)

Fall 2018

a. RTD Pt100 range (22 ~ 190)°C for 5% (0 ~ 3)V

$V_s = 9V$, $R_1 = 200\Omega$, Sensitivity = $0.895mV/^\circ C$ @ $0^\circ C = 10$

22°C ~ 190°C

Ohm range (100 + 23.039) = 108.588 ~ 100 + 190 * 0.39 = 174.16Ω

$R_1 = 200\Omega$ $R_2 = 108.58\Omega$ assume $R_2 = 108.58\Omega$ or 174.1

$R_3 = \frac{R_1 R_2}{R_1} = 200\Omega$ if Bridge

معادلة الجهد

$$R_1 = 200\Omega \quad R_2 = 108.58\Omega \quad R_3 = 200\Omega$$

$$V_0 = 9V \quad V_{0min} = 9 \times \frac{108.58}{200 + 108.58} = 3.16V$$

$$V_{0max} = 9 \times \frac{174.1}{200 + 174.1} = 4.1884V$$


Voltage range (3.16V ~ 4.1884V)

$$O = 3.16mV + offset \Rightarrow M = 2.936502289$$

$$3 = 4.1884mV + offset \quad offset = -9.299399725$$

$$V_0 = 2.936502289 \quad V_0 = 9.299399725$$
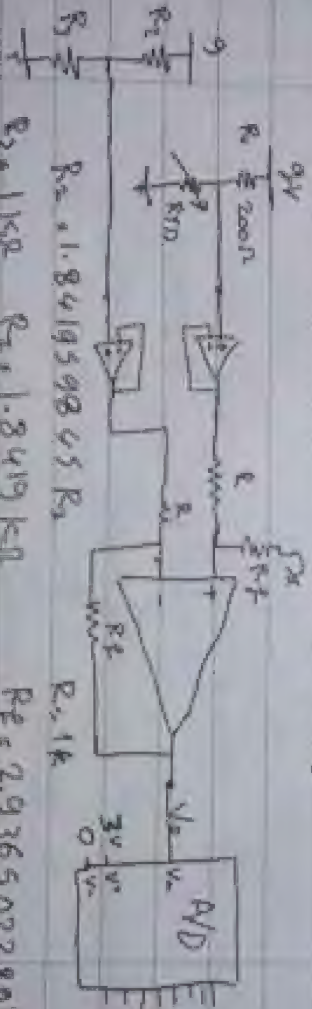
$$V_0 = 2.936502289 (V_{in} - 3.1668287)$$



$$R_2 = 1.841959845k\Omega \quad R_3 = 1k\Omega \quad R_4 = 1.8419k\Omega \quad R_1 = 2.936502289k\Omega$$

$$V_0 = 1.537023320V \Rightarrow D_0 = \frac{V_0}{2.936502289} = 0.5234$$

$$D_0 = 131.16 = 131 \approx 10000011$$



Q13 a-Want is the measuring of simple coded signal and differential signal.

b- Why sometimes we are holding the sampling signal

Q2) Using Temperature sensor (sensitivity = 5mV/C), in the range (30C to 120C), and using voltage to frequency converter VFC (scale factor= 2V/KHz)

$$\frac{2 \sqrt{V}}{1.6 \text{ Ks}}$$

Calculate the sensor output range, and VFC output range.


Using a counter to convert to digital with sampling rate 10 samples/sec, what is the value of the output of the counter if the temperature is 112°C. 75 bits (10 pts)

Q1) Barometer sensor sensitivity is 0.1 mA/bar, used for measuring pressure in the range (4-20 bar) and the value of its output @ 0 bar is 4mA, using 150 Ω Design signal condition circuits for bipolar (8 bit) A/D with voltage reference $\pm 4V$

What is the digital output of ADC at the ~~conversion~~ ^{conversion} time ~~of 2.5~~ ^{of 2.5} ~~ms~~ ^{ms}?

(c) It may be the case, however, that the value of α is not constant across all values of β . In fact, we can see from Figure 1 that the value of α increases as β increases.

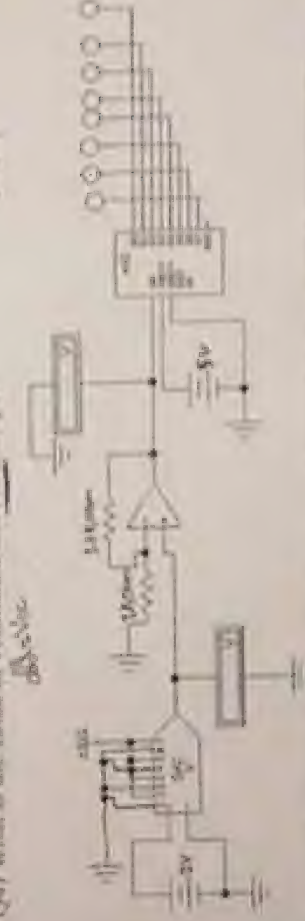0.5) when is the value of voltmeters and A/D output



Q5) a- Using Thermocouple sensor Type J with 40°C reference. What is the value of the current at the temperature 120°C.

b. Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 114°C .


Temperature ($^{\circ}\text{C}$)	η	δ	η	δ
107.5	100.1	100.2	110.1	111.7

2

1000

- Q1) What is the basic elements of a data acquisition system, explain two of them?
Q2) What is the difference between single ended signal and differential signal?
Q3) A length meter range is (0 ~ 5.5m) has quoted inaccuracy of $\pm 2\%$ F.S., what is the maximum measurement error expected for this instrument in centimeter.

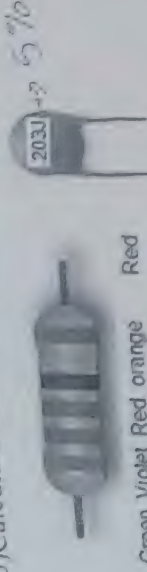- Q4) What is Zero drift and sensitivity drift?
Q5) Calculate the value of the following components:



Green Violet Red orange Red

- Q6) RTD with sensitivity $3\Omega/^\circ\text{C}$, and its value = 320Ω @ 0°C , use wheatstone bridge to calculate its range in volt for temperature range (0 ~ 70°C) . design s.c. circuit for ADC which voltage reference (0 ~ 4V) .


-Get the temperature equation

- Q7) sensitivity of pressure sensor is (2.8 mA/bar) working in the range (0~15bar) , in a noisy area, design a circuit to transmit its data using (4m ~20mA) transmitter , What is the new range in volt of the sensor .


Good Luck

Better 9
Be 8
Right 7
or 6
your 5
Best 4
guess 3
goes 2
Very 1
Wrong 0

A. B $\times 10^c$

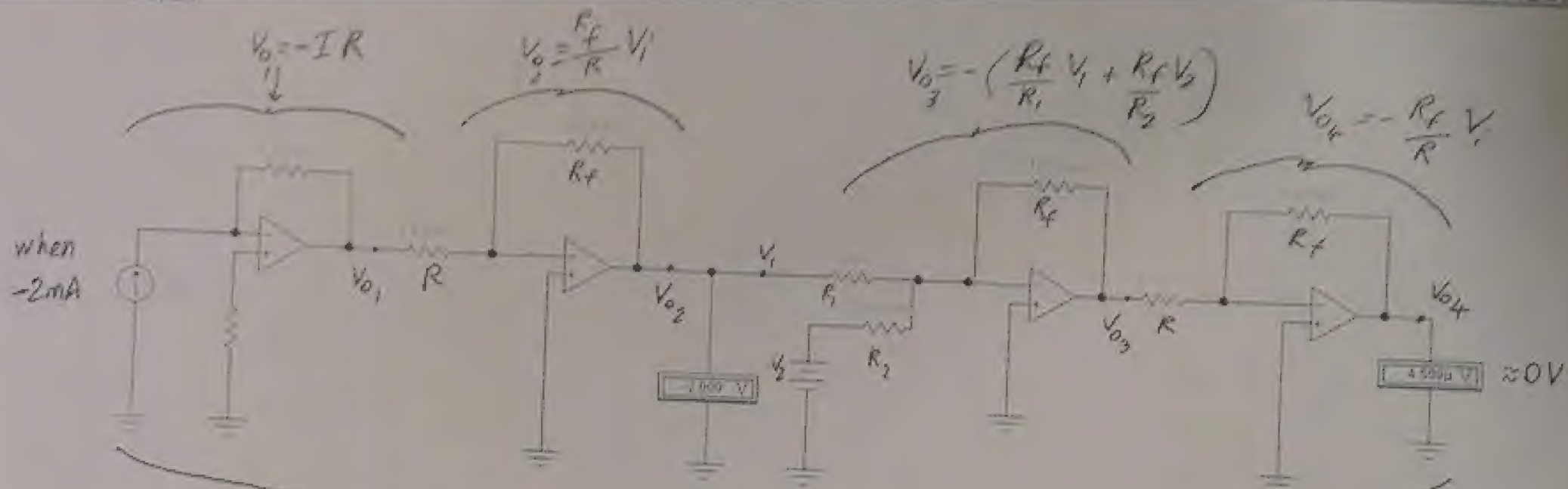

$$V_0 = V_i(0.75) + 1.5$$

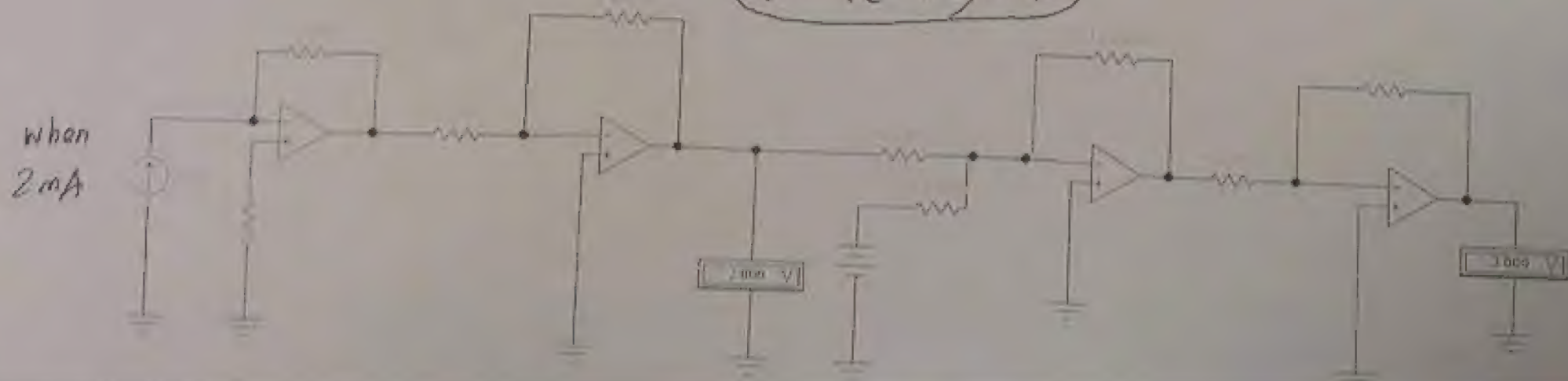

Q. Accelerometer sensitivity 0.2 mV/g
calculate its output range in

(+log) - Design signal conditioning

circuit for $(0 \sim 3V)$ ADC

range $(2 \sim 2 \text{ mA})$
 $(0.2 \times 10 \sim 0.2 \times 10 \text{ mA})$
 $(-2 \sim 2 \text{ V})$ ~~1.50/5/50/5~~

(1K) ~~90/5/50/5~~

$$0 = -2M + \text{offset}$$

$$3 = 2M + \text{offset}$$

$$3 = 4M$$

$$M = \frac{3}{4}$$


$$V_o = V_i M + \text{offset}$$
$$= V_i (0.75) + 1.5$$

V_i	-2V	0	2V
V_o	0	1.5	3

ANS(Q2)

لقد تم الحل

1K

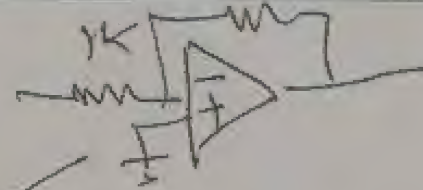


$$V_{01} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

transmitter
 $V_{02} = 2 \times V_{01}$

Buffer
Hi i/p impedance

$$V_{03} = -\frac{R_f}{R} (V_1 - V_2)$$

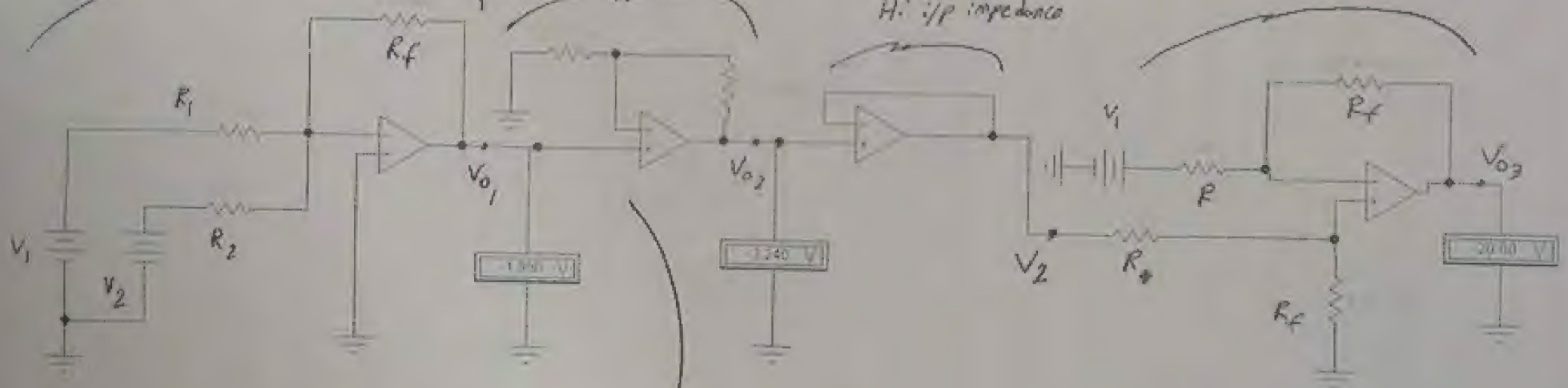

الحل
الاجابة (1ms)

Q2 Sensitivity $0.1V/g$ rang (0~8g) m/s^2
 we want to signal

Condition data for converter to
 use it for (0~5) ADC

$$0 = 1M + offset$$


$$5 = 1.8M + offset$$

$$5 = 0.8M \Rightarrow M = \frac{5}{0.8} = 6.25$$

$$offset = -6.25$$

$$V_o = V_i \cdot 6.25 - 6.25 = 6.25(V_i - 1)$$

V_i	1	1.4	1.8
V_o	0	2.5	5

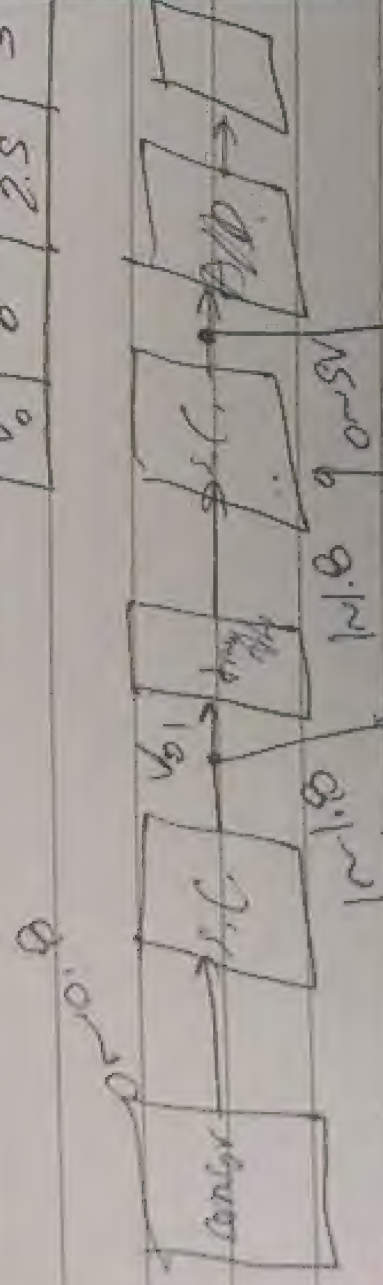

$$V_{02} = 6.25(V_i - 1)$$

$$5 = 1.8V + offset$$

$$V_{01} = V_i + 1$$

Q4) Temperature sensor sensitivity is $452\text{ }^{\circ}\text{C}^{-1}$ in the range (-25°C) and its value at 0°C is $250\text{ }^{\circ}\text{C}^{-1}$. Using Wheatstone bridge convert its range to volts and send its value using 4mA 20mA transmitter) and prepare it for 8bit ADC with voltage reference 0.5Vref .
a) What is the digital output of ADC at the temperature -2°C (12 pts)

Q2) Accelerometer sensor sensitivity is 0.53mA/g , used for measuring Acceleration in the range (-20g) . Design signal condition circuits for bipolar (8 bit) ADC with voltage reference 4V .

- a) What is the digital output of ADC at the acceleration is -3g (12 pts)
b) What is the acceleration when the digital output is 0631

Q3) Design the signal conditioning circuitry to connect the sensor to 10 bit ADC with voltage reference (0.5V) , where sensor output range $(-150 \div 150\text{ mV})$ with frequency 15kHz , Noise signal 20mV with frequency 150Hz , and design filter that Attenuate the noise signal to $2\mu\text{V}$, and taking in account the effect of the filter on the sensor signal (10 pts)

Q4) Using Horowitz-Murphyman type 1 with 0.5V reference find the value of its output at 32°C . The system is to operate under if the temperature is more than 32°C , and using BJT with the following table using linear approximation of resistance versus temperature, find the value of the BJT at 33°C and design circuit operate heater if the temperature is less than 33°C . (12 pts)

Temperature $(^{\circ}\text{C})$	R_{BJT}	β	V_{BE}	V_{CE}	I_{C}
30°C	100Ω	100	0.6V	10V	1mA

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw a you want) (10 pts)

Good Luck (7/2/2018)

Q1) Temperature sensor sensitivity is $0.42\text{mV}/^{\circ}\text{C}$, used for temperature range ($\pm 50^{\circ}\text{C}$). Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 5\text{V}$.

a) What is the digital output of ADC at the temperature 31°C , $\pm 20^{\circ}\text{C}$.

b) What is the temperature when the digital output is B6H. (10 po)

Q2) Design the signal conditioning circuit to connect the sensor to 8 bit ADC with voltage reference $(0-10\text{V})$, where: sensor output range $(+100 - +100\text{ mV})$ with frequency 25Hz . Noise signal 25mV with frequency 760Hz , and using filter that Attenuate the noise signal to 20% of its value, and taking in account the effect of the filter on the sensor signal. (10 po)

Q3) Using pressure sensor with sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\text{mV}/^{\circ}\text{C}$ and its value at zero $^{\circ}\text{C}$ is 300mV . Design circuit which open valve when the pressure is more than 150bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. (10 po)

Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C , and 10°C . Where: sensor sensitivity $-15\text{mV}/^{\circ}\text{C}$, analog output at 0°C is 100mV , sensor range is 50°C . (10 po)



- Q1) a-Using RTD PT100 for temperature range (22°C to 100°C) design a signal conditioning circuit for (0-5V) ADC / use voltage divider circuit, $V_R = 9V$, $R = 200\Omega$
 b-If we will send the sensor output for a distance with same voltage reference.
 c-What is the ADC digital output if the temperature is 15°C.
 d-What is the temperature if the ADC output is (10011101)

$$red = 2V_{(14\text{ bits})}$$

- Q2) Using Acceleration sensor (sensitivity = 0.14mA/g) with offset $7\text{mA @ } 0g$, for the range ($\pm 30g$) and using voltage to frequency converter VFC (scale factor = $4V/\text{mKHz}$).
 a-Draw the block diagram of the operation.
 b-Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.25Sec.

- c-What is the value of the output of the counter if the acceleration is $0.5g$. (10 pts)

- Q3) Barometer sensor sensitivity is 5mV/hPa , and $50\Omega/\text{cm}$ pot. level sensor for (50cm range used for measuring level ($V_R = 9V$ use, $R = 150\Omega$), Design) circuit to turn ON green LED if (level more than 70cm and pressure less than 5bar), red LED if one of them opposite these values. (10 pts)

- Q4) What is the value of voltmeters and ADC and DAC outputs. (8 pts)



- Q5) a- Using Thermocouple sensor Type K, with $0C$ reference, What is the value of temperature if the output is 19mV , What is its output at the temperature $500C$ (4pts)

12069 (3) 13 P 3 3.1

University of Tripoli - Faculty of Engineering
Electrical & Electronic Engineering Department
Final Exam Time: 3 hr Spring 2017

EE 463

5.2.2019

Q1) Temperature sensor sensitivity is $40 \mu V/^\circ C$, in the range $(\pm 25^\circ C)$ and its value at $0^\circ C$ is $280 \mu V$. Using Wheatstone bridge convert its range to volt, and send its value using $4-20 mA$ transmitter) and prepare it for 8bit ADC with voltage reference $0-5V_{ref}$.
a) What is the digital output of ADC at the temperature $-2^\circ C$ [12 pts]

Q2) Accelerometer sensor sensitivity is $0.33 mA/g$, used for measuring Acceleration in the range $(\pm 20 g)$. Design signal condition circuit for bipolar 8 bit ADC with voltage reference $\pm 4V$.

- a) What is the digital output of ADC at the acceleration is $-3 g$ [12]
b) What is the acceleration when the digital output is $06H$. [4] [12 pts]

Q3) Design the signal conditioning circuitry to connect the sensor to 10 bit ADC with voltage reference $(0-5V)$, where: sensor output range $(-150 \sim +150 mV)$ with frequency $15Hz$, Noise signal $20mV$ with frequency $150Hz$, and design filter that Attenuate the noise signal to 25% , and taking in account the effect of the filter on the sensor signal. [10 pts] $V_s = 12.48 \pm 3.5$

Q4) Using Thermocouple sensor Type J with $0^\circ C$ reference, find the value of its output at $32^\circ C$. Design circuit to operate cooler if the temperature is more than $32^\circ C$, and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at $13^\circ C$ and design circuit operate heater if the temperature is less than $13^\circ C$. [12 pts] $R_{TD} = 110 \Omega$
 $V_{ref} = 1.016$

Temperature ($^\circ C$)	4	5	18	25	29
Resistance (Ω)	107.5	108.1	110.2	111.1	111.7

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Levered)

Q1) a-What is the meaning of single ended signal, differential signal and give example.

b- What is sample and what is hold and when we use them. [6 pts]

Q2) Using Temperature sensor (RTD-PT100) in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R_1=110$, $R_2=120$) and using voltage to frequency converter VFC (scale factor = $10\text{KHz}/1.12V$).

a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.

b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is $110C$. 55K

c- Draw Block diagram of the circuit. [16 pts]

Q3) An accelerometer sensor sensitivity is 0.145mV/g , used for measuring pressure in the range ($\pm 20\text{g}$), and the value of its output @ 0g is 5.2mV , using 190Ω converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

a) Calculate sensor output range (current, voltage, Binary).

b) What is the digital output of ADC at the acceleration is 8g .

c) What is the value of acceleration when the digital output is $0D1192H$. [15 pts]

d) If the frequency of the signal is 120Hz and there is unwanted noise with frequency 15KHz , design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range. [05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 12.4°C .

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	103.6	105.1	106.3	107.1	108.5

[08 pts]

Good Luck (Zeyad)

Q1.a) An alarm light goes ON when a pressure sensor voltage rises above 4.00 V. The pressure sensor outputs 20 mV/kPa and has a time constant of 4.9 s. How long after the pressure rises suddenly from 100 kPa to 400 kPa does the light go ON?

Q1.b) A load cell is calibrated at $21\epsilon^a$ and has the following deflection/load characteristic:

Load(kg)	0	50	100	150	200
Deflection (mm)	0	1	2	3	4

When used at $35\epsilon^a$, its characteristic changes to the following:

Load(kg)	0	50	100	150	200
Deflection (mm)	0.2	1.3	2.4	3.5	4.6

Determine the sensitivity coefficients

[10 pts]

Q2.a) A measurement signal has a frequency less than 1KHz, but there is unwanted noise at about 1MHz. Design a filter that attenuate the noise to 1% using a capacitor $0.01\mu\text{f}$. What is the effect on the measurement signal at its maximum of 1KHz (give a comment on the result)?

Q2.b) Signal conditioning analysis shows that the following equation must relate output voltage to input voltage: $V_o = 3.35V_i - 2.68$. Design circuits to do this using a differential amplifier? [12 pts]

Q3.a) Using timing diagram, explain the control lines that coordinate the operation of ADCs?

Q3.b) Design a 5-bit weighted-resistor DAC whose full-scale output voltage is -15v. Logic levels are 1=5v and 0=0v. What is the output voltage when the input is 01010?

[10 pts]

$$T = \frac{P}{V_{ref}}$$

Q1) a- Using RTD PT100 for temperature range (27°C to 190°C), design a signal conditioning circuit for (0-3V) ADC (use voltage divider circuit, $V_S = 9V$, $R1 = 200\Omega$).

b- If we will send the sensor output for a distance with same voltage reference.

c- What is the ADC digital output if the temperature is 100°C.

d- What is the temperature if the ADC output is (10011110).

[14 pts]

Q2) Using Acceleration sensor (sensitivity -0.14mA/g), with offset $7\text{mA}@0\text{g}$, for the range ($\pm 30\text{g}$) and using voltage to frequency converter VFC (scale factor $= 4\text{V}/6\text{KHz}$).

a- Draw the block diagram of the operation.

b- Calculate the sensor output range, and VFC output range, digital output of counter if the sampling is each 0.2Sec.

c- What is the value of the output of the counter if the acceleration is -0.5g .


[10 pts]

Q3) Barometer sensor sensitivity is 5mV/bar , and $5\Omega/\text{cm}$ pot. level sensor for 150cm range used for measuring level ($V_S = 9\text{V}$ use, $R1 = 150\Omega$). Design circuit to turn ON green LED if (level more than 70cm) and pressure less than 5bar), red LED if one of them opposite these values.

[10 pts]

Q4) What is the value of voltmeters and ADC and DAC outputs.

[8 pts]

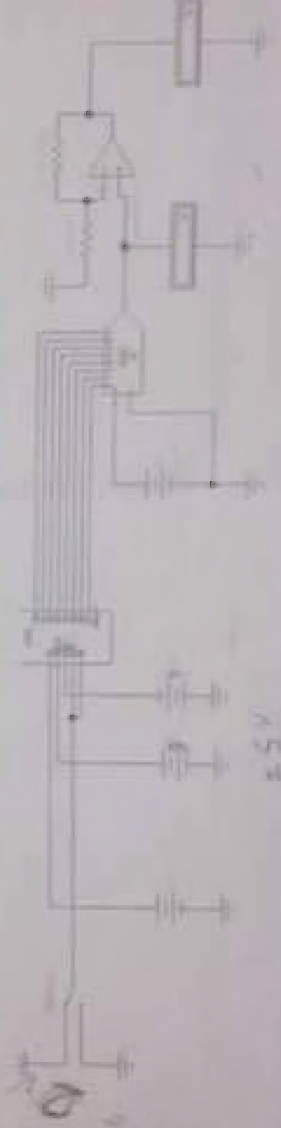

Q5) a- Using Thermocouple sensor Type K with 0°C reference. What is the value of temperature if its output is 19mV. What is its output at the temperature $V_{K19(-40^\circ\text{C})} = ?$.

[8 pts]

Q1) Temperature sensor sensitivity is $0.42\text{mA}/^{\circ}\text{C}$, used for temperature range $(\pm 50^{\circ}\text{C})$.

Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 3\text{V}$.


a) What is the digital output of ADC at the temperature 31°C , -20°C .

b) What is the temperature when the digital output is B6H. (10 pts)

Q2) Design the signal conditioning circuits to connect the sensor to 8 bit ADC with voltage reference $(0-10\text{V})$, where: sensor output range $(-100 \sim +100\text{ mV})$ with frequency 25Hz , Noise signal 20mV with frequency 260Hz , and using filter that Attenuate the noise signal to 20% of its value, and taking in account the effect of the filter on the sensor signal. (10 pts)

Q3) Using pressure sensor which sensitivity is $2.3\text{mV}/\text{bar}$, and temperature sensor which sensitivity is $10\mu\text{V}/^{\circ}\text{C}$ and its value at zero $^{\circ}\text{C} = 300\text{mV}$. Design circuit which open Valve when the pressure is more than 15bar , and operate heater when temperature is less than 20°C , and operate Red LED when both of them are ON. (10 pts)

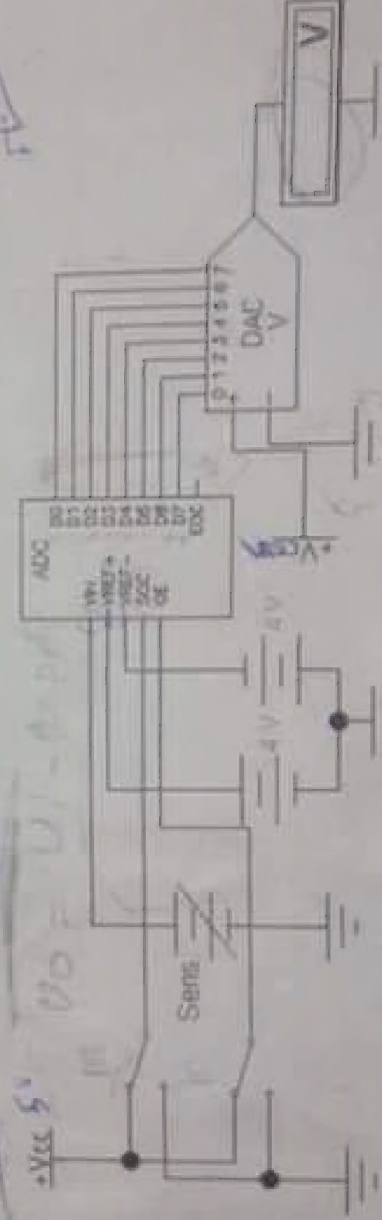Q4) What is the digital value of the ADC output and what is the analog value of DAC output at the temperature 23°C , and -30°C . Where: sensor sensitivity $= 15\text{mV}/^{\circ}\text{C}$, sensor output at $0^{\circ}\text{C} = 100\text{mV}$, sensor range $\pm 50^{\circ}\text{C}$. (10 pts)



Q1) What is the basic elements of a data acquisition system, explain two of them?


Q2) What is the difference between single ended signal and differential signal?

Q3) A length meter range is (0 ~ 5.5m) has quoted inaccuracy of $\pm 2\%$ F.S., what is the maximum measurement error expected for this instrument in centimeter.

Q4) What is Zero drift and sensitivity drift?

$$\begin{aligned} 100\% &= 5.5\text{m} = 550\text{cm} \\ 100000\% &= 55000\text{cm} = 550\text{m} \\ 100\% &= 550\text{cm} \\ 100000\% &= 55000\text{cm} = 550\text{m} \end{aligned}$$

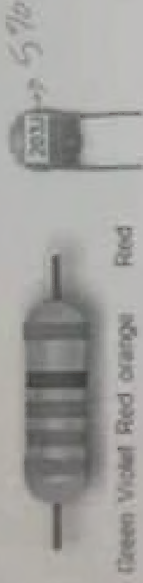Q5) Calculate the value of the following components:



Green Violet Red orange Red

Q6) RTD with sensitivity $3\Omega/^\circ\text{C}$, and its value = 320Ω @ 0°C , use wheatstone bridge to calculate its range in volt for temperature range (0 ~ 70°C), design s.c. circuit for ADC which voltage reference (0 ~ 4V).

-Get the temperature equation

Q7) sensitivity of pressure sensor is (2.8 mA/bar) working in the range (0 ~ 15bar), in a noisy area, design a circuit to transmit its data using (4mA ~ 20mA) transmitter, What is the new range in volt of the sensor.

Good Luck

Better 5
Be 3
Right 7
or 6
your 5
Best 4
guess 3
goes 2
very 1
wrong 0

A. B x 10²